
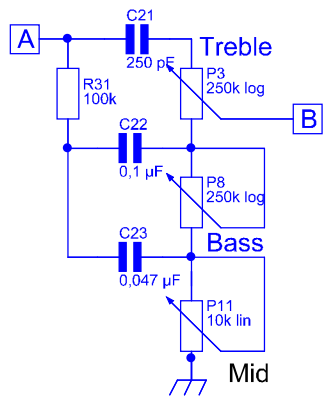


Fender Tone-Stack

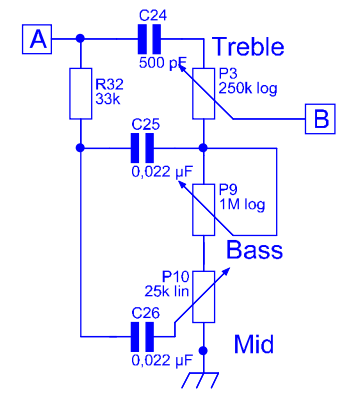

Marshall Tone-Stack




TT66 Mods & Improvements


Mod 1) C-L-C Filter instead of a C-R-C Filter
Using a Hammond 158M Choke instead of a resistor will reduce hum even if the wiring is not very good made

Mod 2) C10
Raise the capacitor C20 from 22μF upto 47μF will reduce the hum a little bit if there is any.

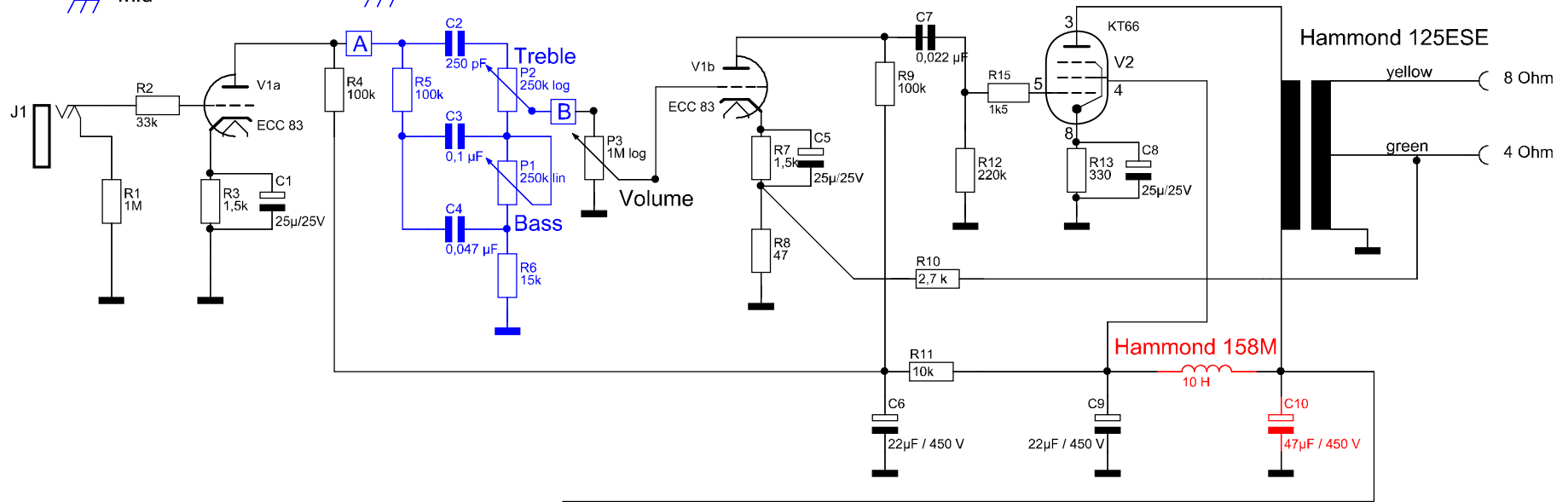Mod 3) Different Tonestacks
The tone-stacks used for the TT-SAM kit can be used here as well. They have to be "plugged" in between point [A] :



Hammond 372BX

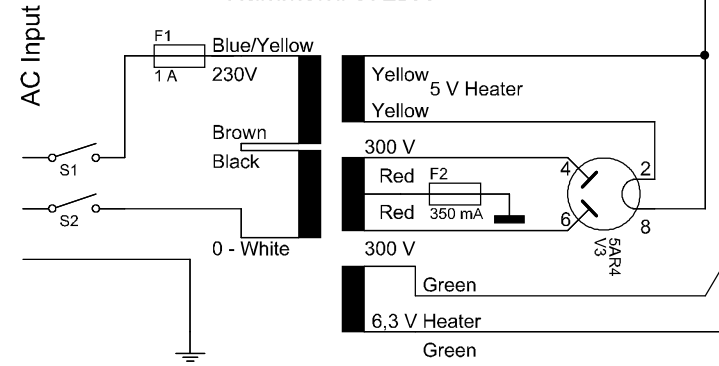

R13: 470 Ohm for 6V6 Powertube

Änderungen			Datum	Name	Bezeichnung	Blattzahl:
Datum	Name	gez.:			TT66 Mods & Improvements	1
		gepr.:				Blatt-Nr.:
					Zeichnungs-Nr.:	1