


Switching logic Badder Cat V1.0 26.10.2012

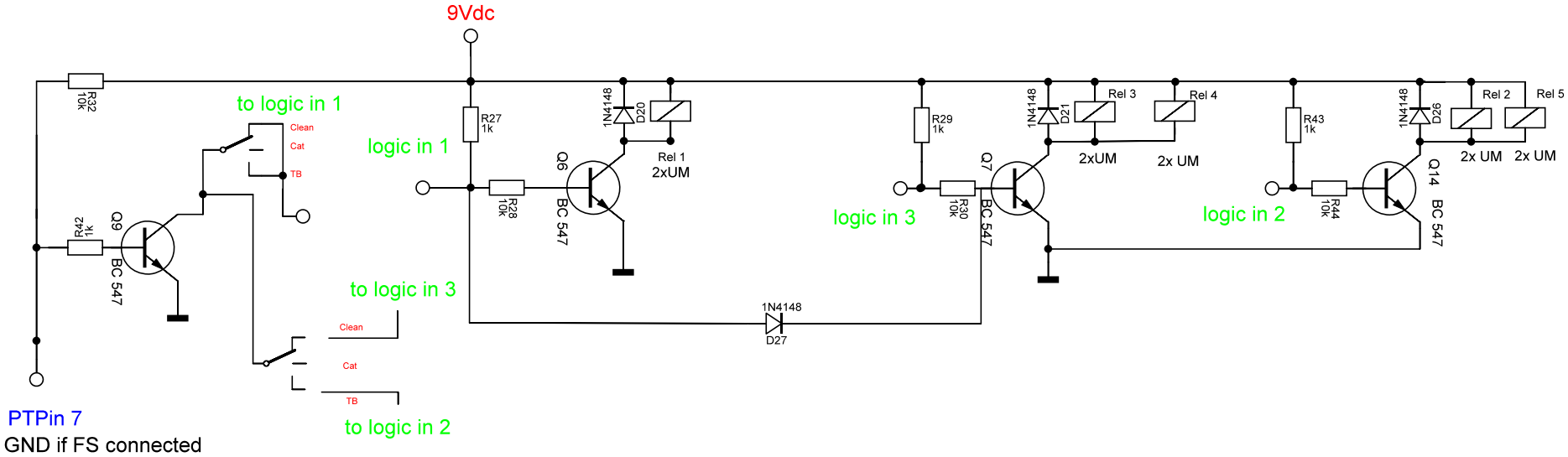


PTPin 7
GND if FS connected

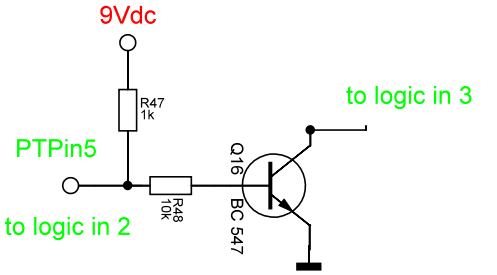

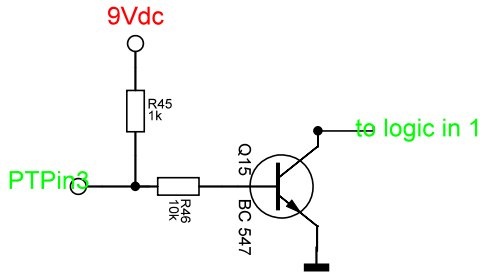

	logic in1	logic in2	logic in3
Clean	low	high	low
TB	low	low	high
Cat	high	high	high

	Rel1	Rel2	Rel3	Rel4	Rel5
Clean	low	high	low	low	-
TB	low	low	high	high	low
Cat	high	high	high	high	high

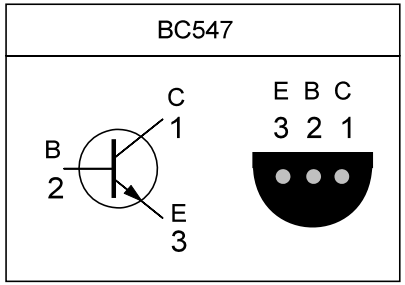

If "logic in" is high (V+) -> BC547 switches (output is low)
-> relais switches (high)